

EXPERIMENT I: MSI COMPONENTS

DECODER

W	X	Y	Z	M0	M1	M2	M3	M4	M5	M6	M7	M8	M9	M10	M11	M12	M13	M14	M15
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1

Figure 1 4x16 Decoder truth table

```
`timescale 1ns / 1ps
```

```
module DECODER(input [3:0]IN, output reg [15:0]OUT);
```

```
always @(*)
```

```
begin
```

```
case(IN)
```

```
4'b0000 : OUT=16'b0000000000000001;
```

```
4'b0001 : OUT=16'b0000000000000010;
```

```
4'b0010 : OUT=16'b00000000000000100;
```

```
4'b0011 : OUT=16'b00000000000001000;
```

```
4'b0100 : OUT=16'b00000000000010000;
```

```
4'b0101 : OUT=16'b00000000000100000;
```

```
4'b0110 : OUT=16'b00000000001000000;
```

```
4'b0111 : OUT=16'b00000000010000000;
```

```
4'b1000 : OUT=16'b00000000100000000;
```

```
4'b1001 : OUT=16'b000000010000000000;
4'b1010 : OUT=16'b000000100000000000;
4'b1011 : OUT=16'b000001000000000000;
4'b1100 : OUT=16'b000010000000000000;
4'b1101 : OUT=16'b001000000000000000;
4'b1110 : OUT=16'b010000000000000000;
4'b1111 : OUT=16'b100000000000000000;
endcase
end
endmodule
```

```
`timescale 1ns / 1ps
module top_module( sw , btn, led, seg, dp, an);
input [7:0]sw;
input [3:0]btn;
output [7:0] led;
output [6:0] seg;
output dp;
output [3:0] an;
DECODER decoder1( sw[3:0], {dp, seg, led} );
assign an = 4'b1110;
endmodule
```

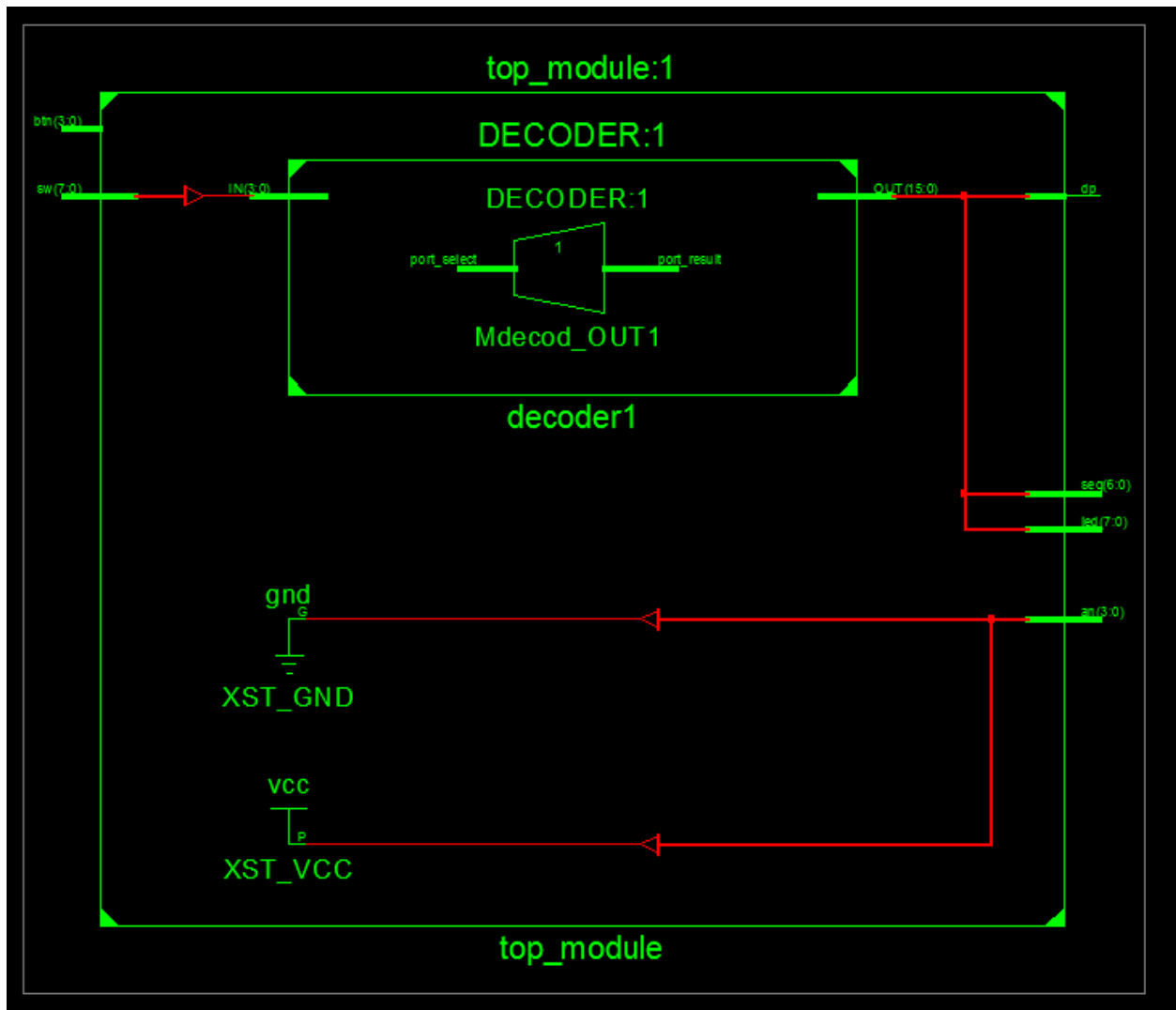


Figure 2 Decoder RTL Schematics

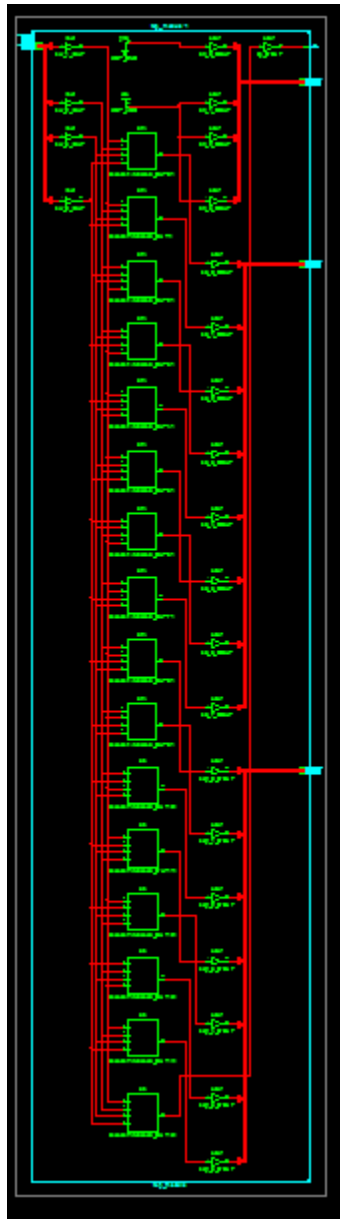


Figure 3 Technology Schematics of decoder as whole

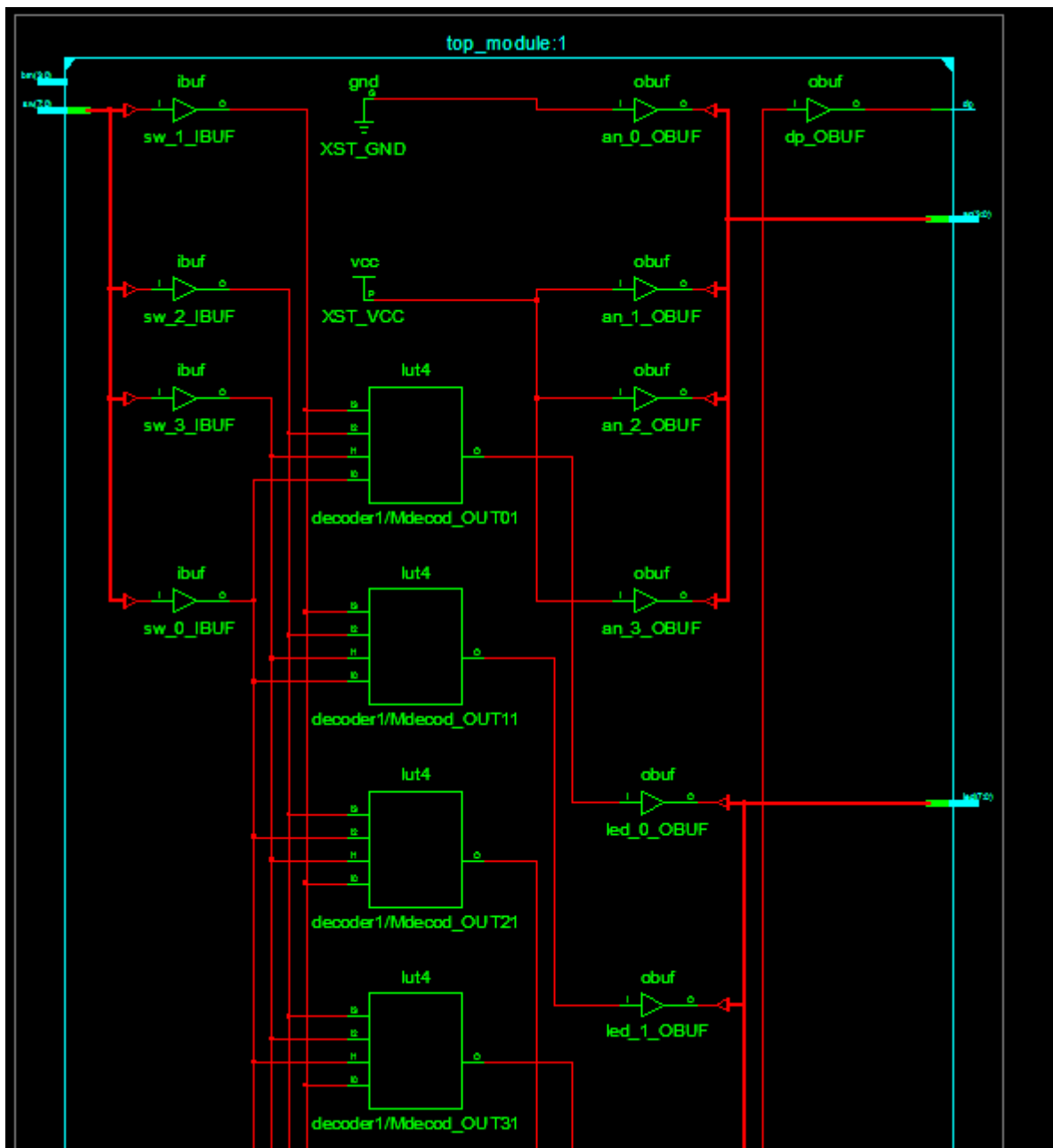


Figure 4 A part of Technology Schematics of decoder

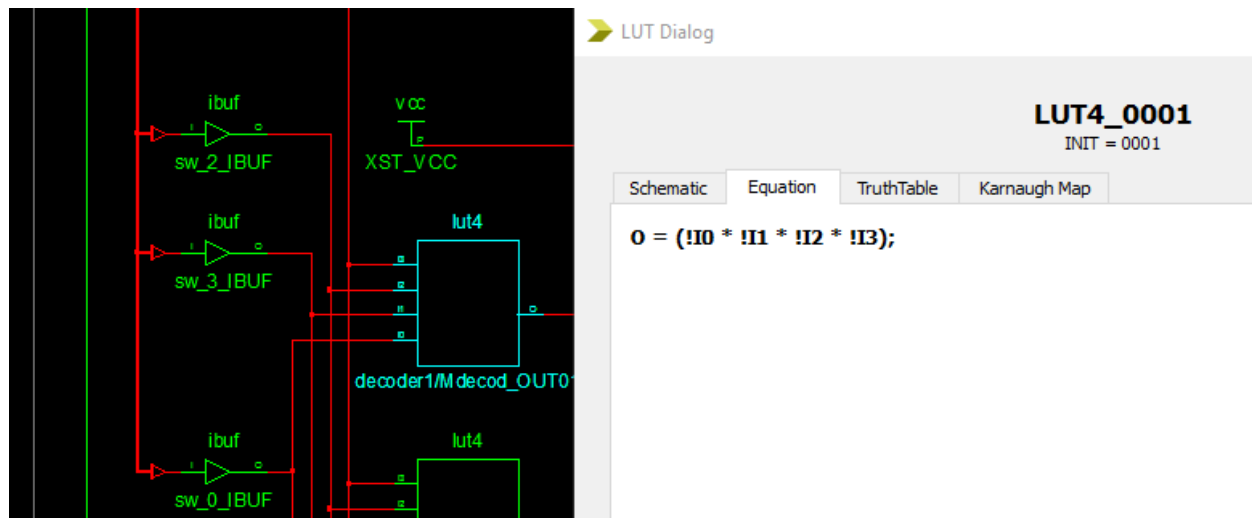


Figure 5 LUT equation of Decoder

It used 16 LUTs to complete decoder. When we change the switch, the inputs are changing. It uses switches to give our output.

sw<2>	led<3>	8.332
sw<2>	led<4>	8.297
sw<2>	led<5>	7.106
sw<2>	led<6>	10.456
sw<2>	led<7>	12.393
sw<2>	seg<0>	7.239
sw<2>	seg<1>	7.238
sw<2>	seg<2>	8.673

Figure 6 Part of delay table

Greatest delay is from switch 3 to led 7 which is 12.393 ns.

 


Figure 7 Layout of decoder on FPGA Editor

After adding time constraint 10 ns, greatest delay is from switch 3 to led 6 with 9.809 ns.

sw<2>	led<5>	7.373
sw<2>	led<6>	9.809
sw<2>	led<7>	8.799
sw<2>	seg<0>	7.538
sw<2>	seg<1>	7.156
sw<2>	seg<2>	7.653

Figure 8 Part of delay table

 


Figure 9 Layout of decoder with time constraint on FPGA Editor

Layout became more orderly to accomplish the 10ns constraint. The decoder without time constraint used any place on FPGA.

PRIORITY ENCODER

Inputs				Outputs		
D_0	D_1	D_2	D_3	Y_1	Y_0	V
0	0	0	0	×	×	0
1	0	0	0	0	0	1
×	1	0	0	0	1	1
×	×	1	0	1	0	1
×	×	×	1	1	1	1

Figure 10 Priority encoder truth table

 


Figure 11 Priority encoder Karnaugh map and output

```

module ENCODER(IN, E, OUT);
input [3:0]IN;
output [1:0]OUT;
output E;
wire in2_not, d1xd2_not;
NOT not1(IN[2], in2_not);

```

```

AND and1(IN[1],in2_not,d1xd2_not);
OR or1(IN[3],d1xd2_not,OUT[0]);
OR or2(IN[2],IN[3],OUT[1]);
wire y0,y1;
OR or3(IN[0],IN[1],y0);
OR or4(IN[2],IN[3],y1);
OR or5(y0,y1,E);
endmodule

```

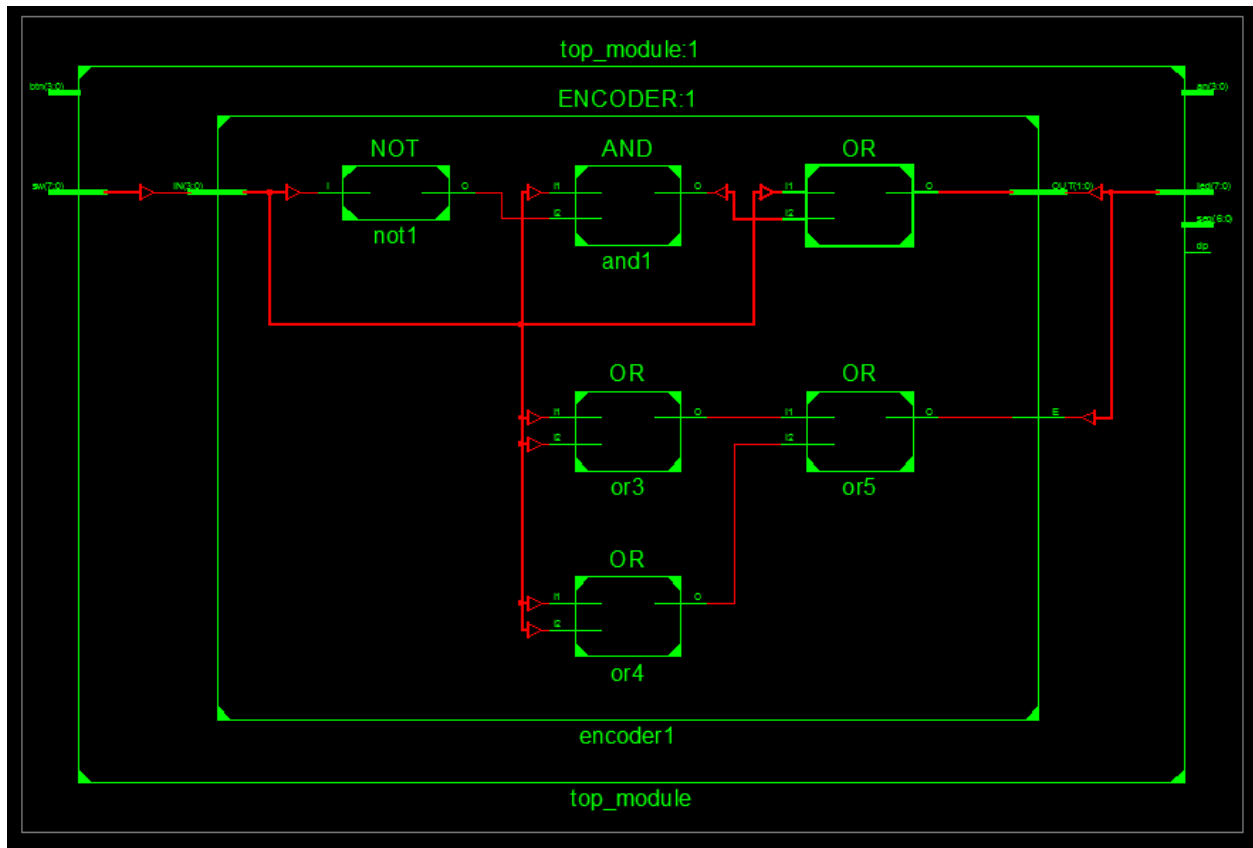


Figure 12 RTL schematics of priority encoder

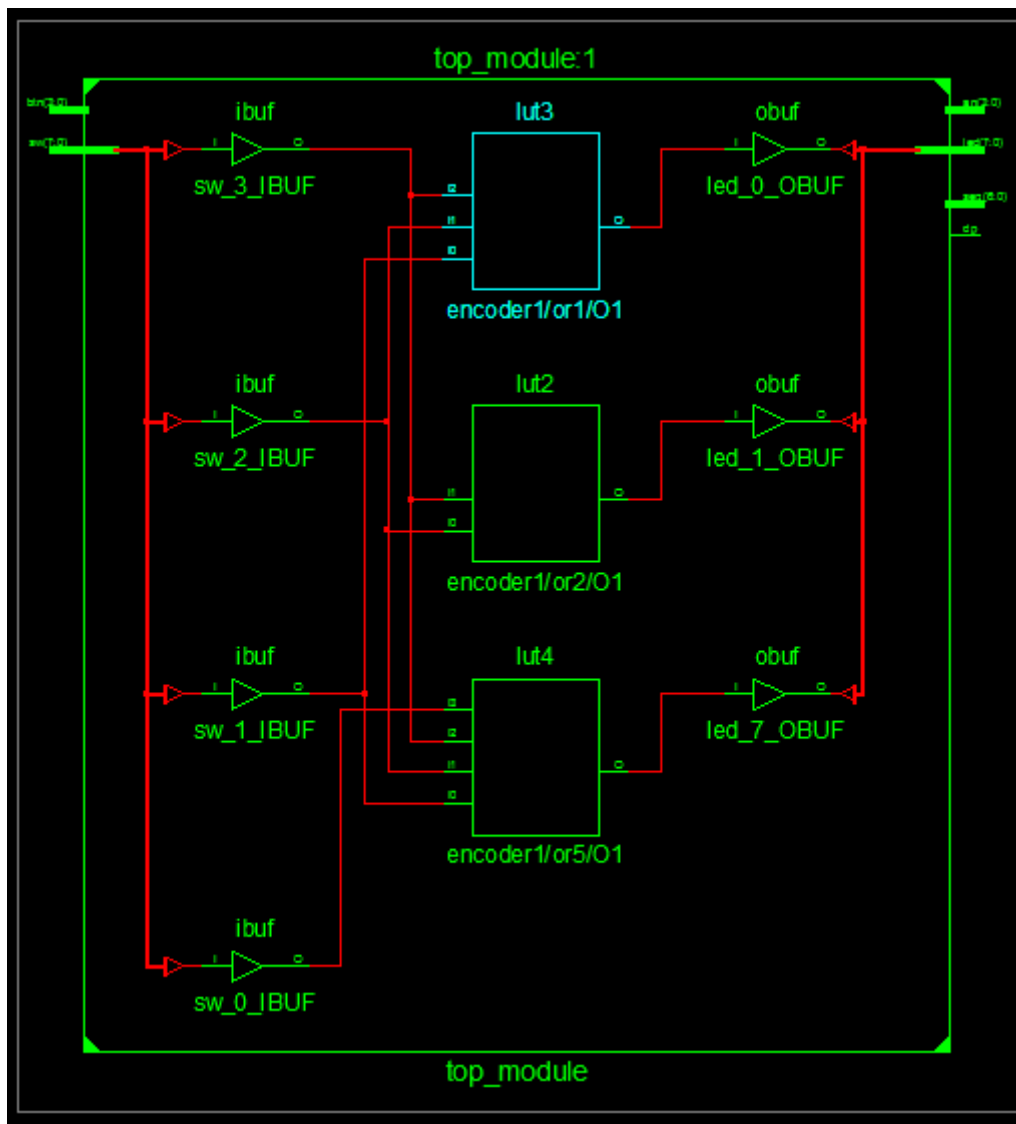


Figure 13 Technology schematics of priority encoder

Technology schematics have 3 LUTs but RTL schematics only have gates.

 


Figure 14 Layout of priority encoder on FPGA Editor

MULTIPLEXER

```

module MUX(D,S,O);
input [3:0]D;
input [1:0]S;
output O;
wire w0,w1,w2,w3;
assign w0 = (~S[0])&(~S[1])&D[0];
assign w1 = S[0]&(~S[1])&D[1];
assign w2 = (~S[0])&S[1]&D[2];
assign w3 = S[0]&S[1]&D[3];
assign O = w0|w1|w2|w3;
endmodule

```

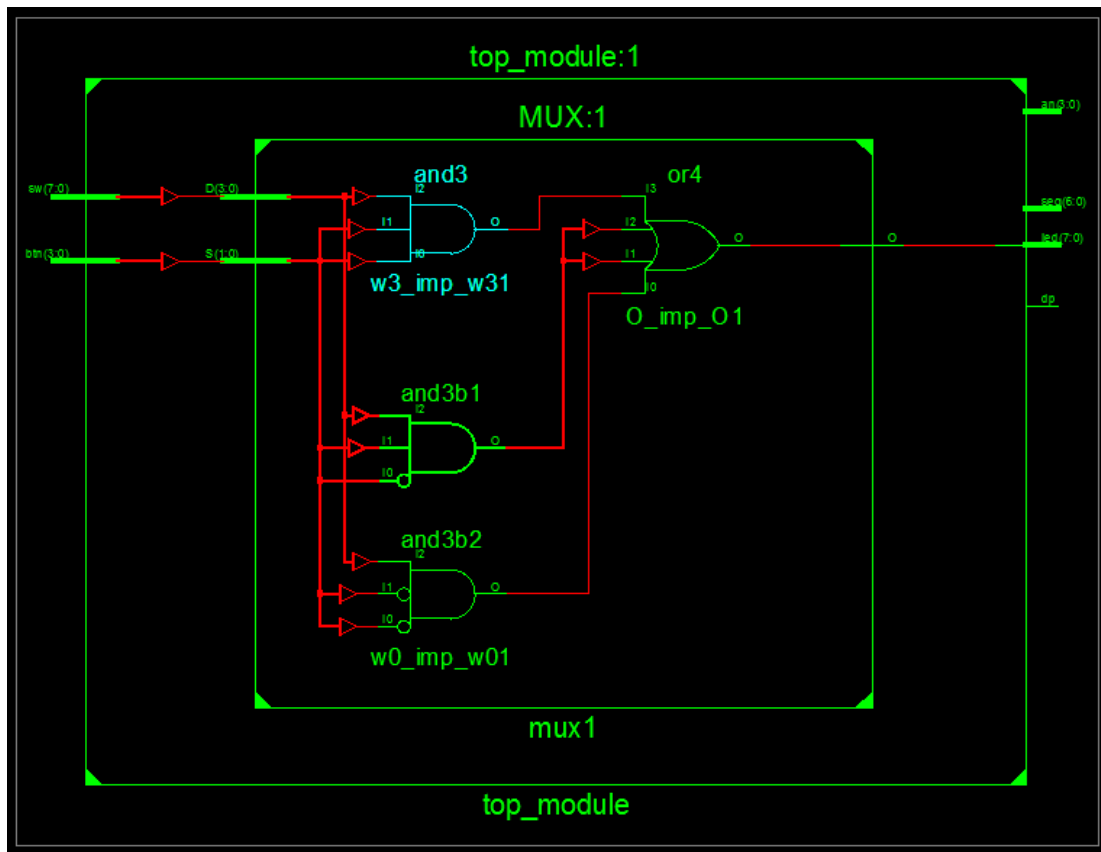


Figure 15 RLT schematics of multiplexer

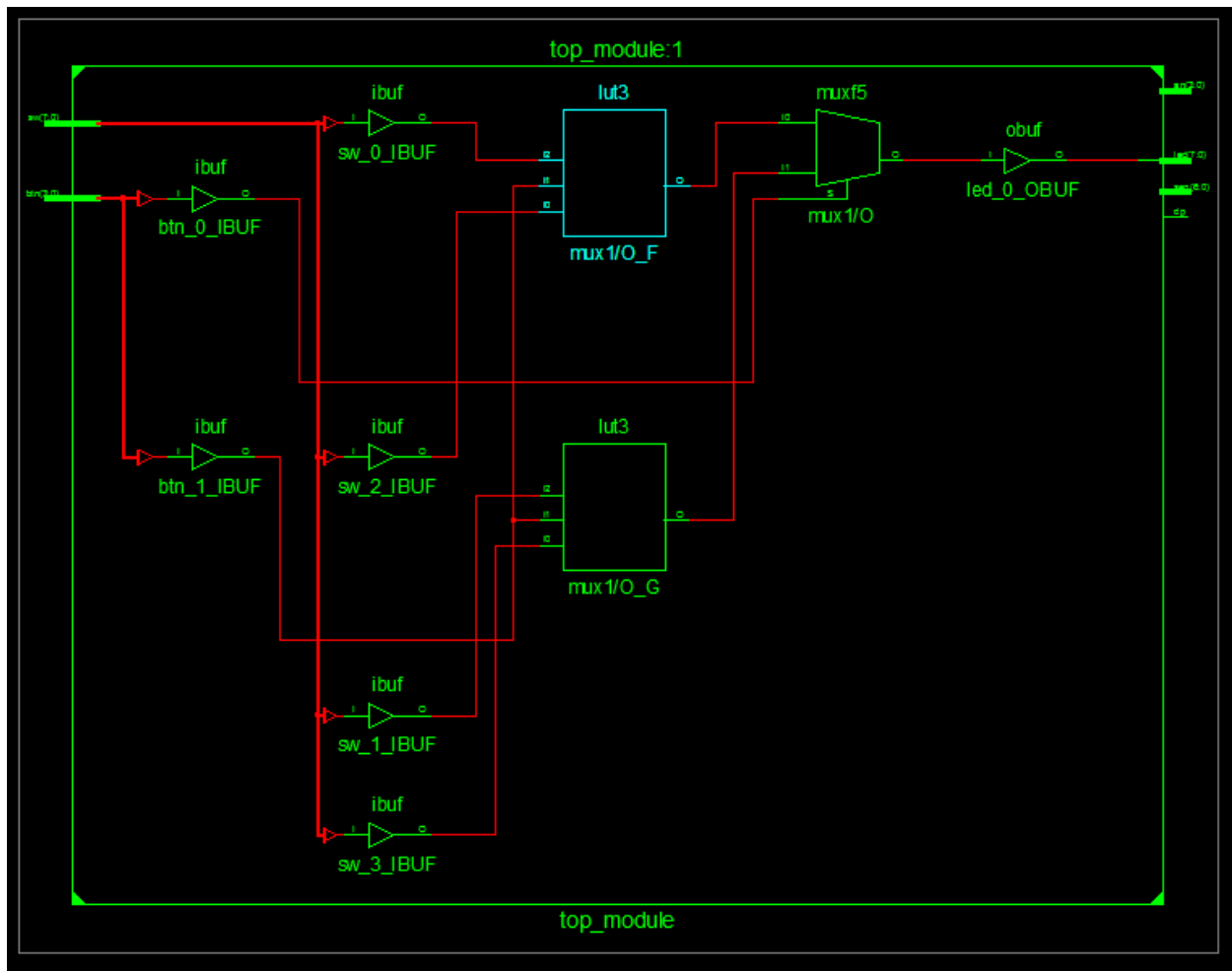


Figure 16 Technology schematics of multiplexer

 


Figure 17 Multiplexer part in the technology schematics

 


Figure 18 Layout of multiplexer in FPGA Editor

DEMULTIPLEXER

```
module DEMUX(D,S,O);  
input D;  
input [1:0]S;  
output [3:0]O;  
wire n0,n1,o0,o1,o2,o3,z0,z1,z2,z3;  
NOT not1(S[0],n0);  
NOT not2(S[1],n1);  
AND and1(n0,n1,z0);  
AND and2(S[0],n1,z1);  
AND and3(n0,S[1],z2);  
AND and4(S[0],S[1],z3);  
TRI trI1(D,z0,O[0]);  
TRI trI2(D,z1,O[1]);  
TRI trI3(D,z2,O[2]);  
TRI trI4(D,z3,O[3]);  
endmodule
```

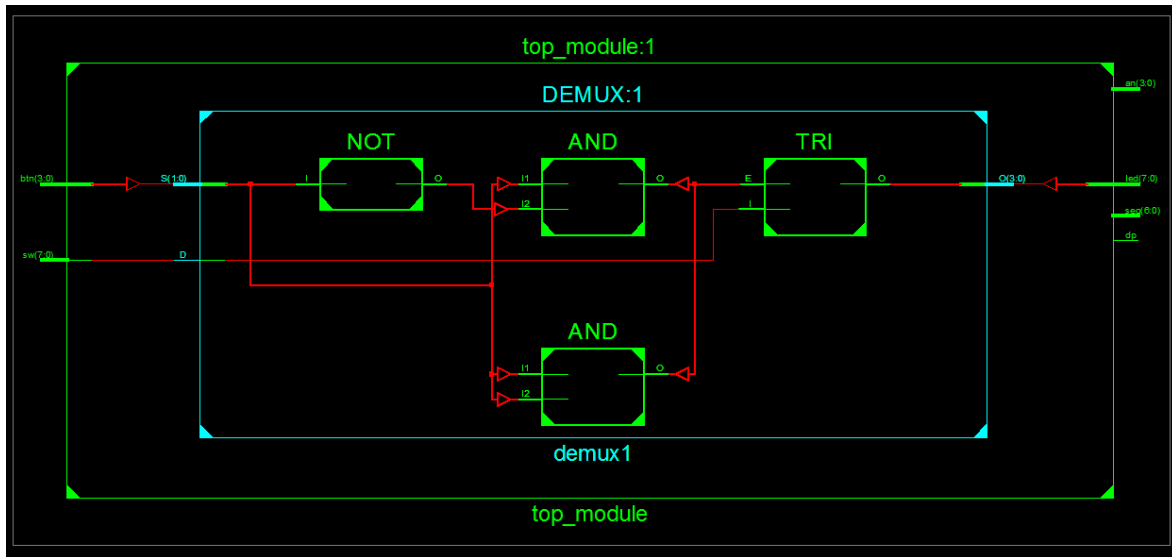


Figure 19 RTL schematics of demultiplexer

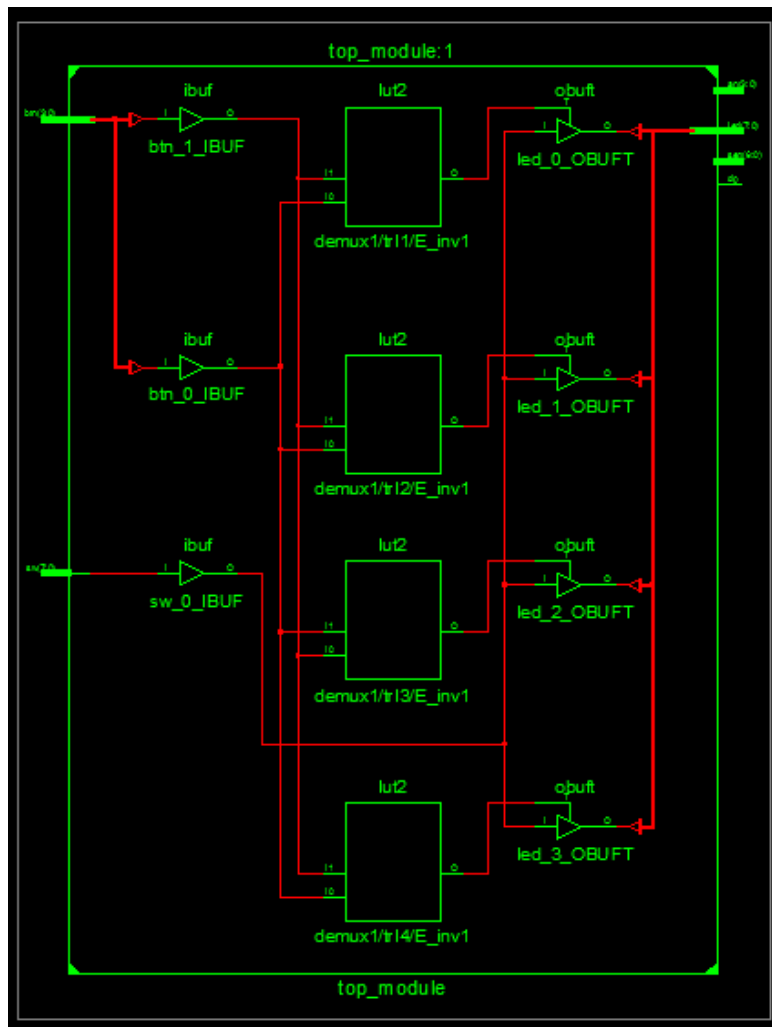


Figure 20 Technology schematics of demultiplexer

LUTs in the technology have OR gates and NOT gates in them. We pick which LUT will work with buttons on FPGA.

 


Figure 21 Layout of demultiplexer in FPGA Editor

Demultiplexer's outputs have faster response rate than others. Because its inputs are coming from near. However, its slew rate is slow.

ALWAYS CASES

```
module MUX(D,S,O);  
input [3:0]D;  
input [1:0]S;  
output O;  
reg O;  
always @( D )  
begin  
    case ( S )  
        2'd0 : O = D[0];  
        2'd1 : O = D[1];  
        2'd2 : O = D[2];  
        2'd3 : O = D[3];  
        default : O = 1'bx;  
    endcase  
end  
endmodule
```

Data Sheet report:

All values displayed in nanoseconds (ns)

Pad to Pad

Source Pad	Destination Pad	Delay
btn<0>	led<0>	8.145
btn<1>	led<0>	7.894
sw<0>	led<0>	7.423
sw<1>	led<0>	6.926
sw<2>	led<0>	7.344
sw<3>	led<0>	7.562

Figure 22 Delays of pads in mutiplexer with always and case

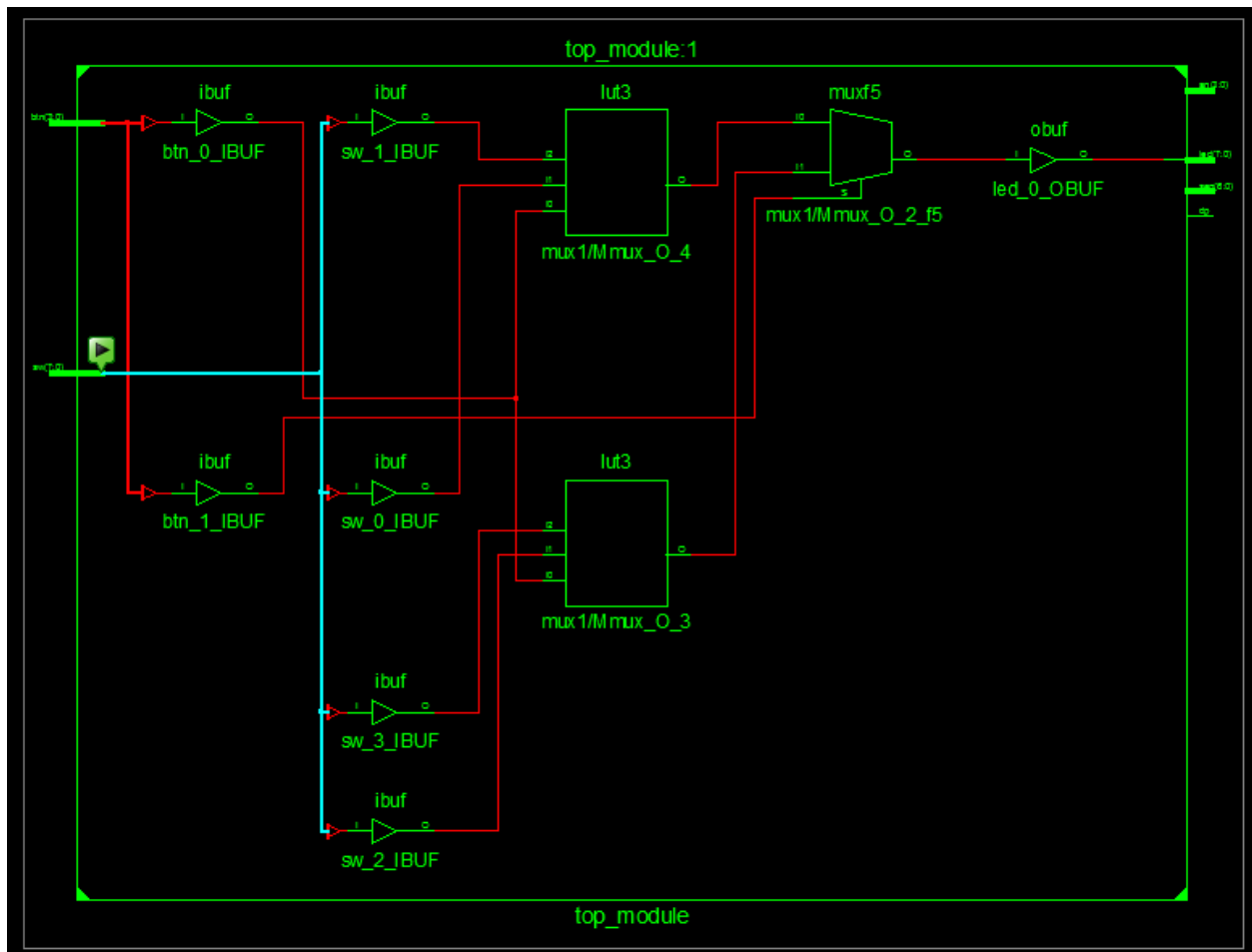


Figure 23 Technology schematics of multiplexer with always and case


```
module ENCODER(IN, E,OUT);  
input [3:0]IN;  
output [1:0]OUT;  
output E;  
reg[1:0]OUT;  
reg E;  
always @(IN)  
begin  
case(IN)  
    4'b1XXX: OUT= 2'b11;  
    4'b01XX: OUT= 2'b10;  
    4'b001X: OUT= 2'b01;  
    4'b0001: OUT= 2'b00;  
    default: OUT=2'bx;  
  
endcase  
end  
endmodule
```