

# Project 1 COMBINATIONAL CIRCUITS

## PROJECT LIST

1. Design a combinational circuit which realizes  $y = \sin(x)$  function. **x input** is going to be 9-bits wide, and it is going to take value of degrees in the interval  $[0,360)$ . **y output** is going to be 6-bits, and it is going to be represented in 2's complement representation and it will be fixed-point with 2 digits decimal and 4 digits fractional. Y output is going to be in the interval  $[-1,1]$ .
2. Design a combinational circuit which realizes  $y = \cos(x)$  function. **x input** is going to be 9-bits wide, and it is going to take value of degrees in the interval  $[0,360)$ . **y output** is going to be 6-bits, and it is going to be represented in 2's complement representation and it will be fixed-point with 2 digits decimal and 4 digits fractional. Y output is going to be in the interval  $[-1,1]$ .
3. Design a combinational circuit which realizes  $y = \tan(x)$  function. **x input** is going to be 7-bits wide, and it is going to take value of degrees in the interval  $[-64,64)$ . **y output** is going to be 6-bits, and it is going to be represented in 2's complement representation and it will be fixed-point with 2 digits decimal and 4 digits fractional. Y output is going to be in the interval  $[-2,2]$ .
4. Design a combinational circuit which realizes  $y = \sinh(x)$  function. **x input** is going to be 7-bits wide, and it is going to take value of degrees in the interval  $[-4,4)$  and it will be fixed-point with 3 digits decimal and 4 digits fractional. **y output** is going to be 10-bits, and it is going to be represented in 2's complement representation and it will be fixed-point with 6 digits decimal and 4 digits fractional. Y output is going to be in the interval  $[-32,32]$ .
5. Design a combinational circuit which realizes  $y = \cosh(x)$  function. **x input** is going to be 7-bits wide, and it is going to take value of degrees in the interval  $[-4,4)$  and it will be fixed-point with 3 digits decimal and 4 digits fractional. **y output** is going to be 10-bits, and it is going to be represented in 2's complement representation and it will be fixed-point with 5 digits decimal and 5 digits fractional. Y output is going to be in the interval  $[0,32]$ .
6. Design a combinational circuit which realizes  $y = \tanh(x)$  function. **x input** is going to be 7-bits wide, and it is going to take value of degrees in the interval  $[-1,1)$  and it will be fixed-point with 1 digit decimal and 6 digits fractional. **y output** is going to be 8-bits, and it is going to be represented in 2's complement representation and it will be fixed-point with 1 digit decimal and 7 digits fractional. Y output is going to be in the interval  $[-1,1]$ .
7. Design a combinational circuit which realizes  $y = 3^x$  function. **x input** is going to be 6-bits wide, and it is going to take values in the interval  $[0,8)$  and it will be fixed-point with 3 digits decimal and 3 digits fractional. **y output** is going to be 13-bits positive integers, and it is going to be in the interval  $[0,8192]$ .
8. Design a combinational circuit which realizes  $y = 2.5^x$  function. **x input** is going to be 6-bits wide, and it is going to take values in the interval  $[0,8)$  and it will be fixed-point with 3 digits decimal and 3 digits fractional. **y output** is going to be 11-bits positive integers, and it is going to be in the interval  $[0,2048]$ .
9. Design a combinational circuit which realizes  $y = \ln(x)$  function. **x input** is going to be 10-bits wide, and it is going to take values in the interval  $[1,1024)$ . **y output** is going to be 8-bits, and it will be fixed-point with 3 digits decimal and 5 digits fractional. Y output is going to be in the interval  $[0,8)$ .
10. Design a combinational circuit which realizes  $y = \log(x)$  function. **x input** is going to be 10-bits wide, and it is going to take values in the interval  $[1,1024)$ . **y output** is going to be 8-bits, and it will be fixed-point with 3 digits decimal and 5 digits fractional. Y output is going to be in the interval  $[0,8)$ .
11. Design a combinational circuit which is a **6x64 multiplexer**. **X input** is going to be 64-bits, **C input** is going to be 6-bits, and **y output** is going to be 1 bit.
12. Design a combinational circuit which is a **demultiplexer**. **X input** is 1-bit, **C input** is 6-bits, and **Y output** is 64-bits. Outputs which are not selected is going to be **high impedance(z)**.
13. Design a combinational circuit which is a **comparator**. Comparator is going to have 10-bits **x input** and 1-bit **y output**. Y output is going to be 1 when x has **three ones** or x has **three zeros**.
14. Design a combinational circuit which is a **comparator**. Comparator is going to have 10-bits **x input** and 1-bit **y output**. Y output is going to be 1 when x has **four ones** or x has **two zeros**.

# Project 1

## COMBINATIONAL CIRCUITS

15. Design a combinational circuit which is a **comparator**. Comparator is going to have 10-bits **x input** and 1-bit **y output**. Y output is going to be 1 when x has **five ones** or x has **a zero**.
16. Design a combinational circuit which is a **comparator**. Comparator is going to have 10-bits **x input** and 1-bit **y output**. Y output is going to be 1 when x has **consecutive two ones** or x has **consecutive five zeros**.
17. Design a combinational circuit which is an **encoder**. Encoder is going to have 15-bits **x input** and 4-bits **y output**. Number of ones in x input is going to be displayed on the y output.
18. Design a combinational circuit which is an **encoder**. Encoder is going to have 14-bits **x input** and 4-bits **y output**. Number of 1 couples which are separated by zero or zeroes is going to be displayed on the y output. (such as 101, 10001, 110011)
19. Design a combinational circuit which is a **comparator**. Comparator is going to have 32-bits **a input**, 32-bits **b input**, and 1-bit **e output**. e output is going to be 1 when a input is greater than b input, and is going to be 0 otherwise. Operators (**<**, **>**, **=**) are not allowed. You will design a 1-bit comparator module, 32-bit comparator will be realized using this 1-bit comparator module.
20. Design a combinational circuit which is **gray encoder**. Gray encoder is going to have 8-bits **x input**, and 8-bits **y output**.

### DIRECTIVES FOR ALL PROJECTS

1. Input values for testbenches are going to be read from a text file, and output values are going to be written into another text file. You can prepare your input text by using MATLAB, C etc.
2. Project report is going to be 2 pages at most.
3. You must explain how your circuit works in your project report.